

Boolean Algebra

Define Boolean Expression

Boolean expressions are the expressions that evaluate a condition and result in a boolean value i.e. true or false.

example ; $a > b \ \&\& \ a > c$ is a boolean expression.
~~true~~ .

Boolean function

~~A function from B^n~~

Let $B = \{0, 1\}$. Then $B^n = \{(x_1, x_2, \dots, x_n) \mid x_i \in B \text{ for } 1 \leq i \leq n\}$

is the set of all possible n -tuples of 0 and 1.
The variable x is called boolean variable if it assumes values only from B .
A function from B^n to B is called a Boolean function.

A function of n degree n if a boolean expression of n variables can specify it.

Find the value of the Boolean expression:

$$F(x, y, z) = xy + \bar{z}$$

The values of this function are displayed in the table.

x	y	z	$\bar{z}$	xy	$xy + \bar{z}$
1	1	1	0	1	1
1	1	0	1	1	1
1	0	1	0	0	0
1	0	0	1	0	1
0	1	1	0	0	0
0	1	0	1	0	1
0	0	1	0	0	0
0	0	0	1	0	1

* law 851 page 9.
prove the absorption law, $x(x+y) = x$

L.H.S.

$$x(x+y)$$

$$= (x+0)(x+y)$$

[Identity law for the Boolean sum]

$$= \cancel{(x+0)}y$$

$$= x+0 \cdot y$$

[Distributive law of Boolean Sum over the Boolean product]

$$= x+y \cdot 0$$

[Commutative law for Boolean product]

$$= x+0$$

[Domination law for Boolean product]

$$= x$$

[Identity for Boolean sum]

R.H.S. (proved)

Find the boolean product of $A = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$, $B = \begin{bmatrix} 1 & 1 & 0 \\ 0 & 1 & 0 \end{bmatrix}$

$$A \odot B = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \odot \begin{bmatrix} 1 & 1 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} (1 \wedge 1) \vee (0 \wedge 0) & (1 \wedge 1) \vee (0 \wedge 1) & (1 \wedge 0) \vee (0 \wedge 0) \\ (0 \wedge 1) \vee (1 \wedge 0) & (0 \wedge 1) \vee (1 \wedge 1) & (0 \wedge 0) \vee (1 \wedge 0) \end{bmatrix}$$

$$= \begin{bmatrix} 1 \vee 0 & 1 \vee 0 & 0 \vee 0 \\ 0 \vee 0 & 0 \vee 1 & 0 \vee 0 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 1 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

Define Duality.

Duality states that the dual of a Boolean expression is obtained by interchanging Boolean sums and Boolean products and interchanging 0s and 1s.

Find the dual of $x(y+0)$ and $x.1+(\bar{y}+z)$

The dual can be obtained by interchanging sum and product and interchanging 1 and 0.

$\therefore x(y+0)$ becomes $\bar{x}+(y.1)$

$\bar{x}.1+(\bar{y}+z)$ becomes $(\bar{x}+0)(\bar{y}.z)$

Define Boolean Algebra:

What do you mean by SOP and POS?

SOP:

SOP stands for sum of product. SOP form is a set of product terms that are summed together. It is also known as min term.

POS:

POS stands for product of sum. POS form is a set of sum terms that are producted together. It is also known as max term.

Find the SOP expansion

$$F(x, y, z) = (x+y)\bar{z}$$

We can construct the SOP expansion by determining the values of F for all possible values of the variable x, y and z .

x	y	z	$\bar{z}$	$x+y$	$(x+y)\bar{z}$
1	1	1	0	1	0
1	1	0	1	1	1
1	0	1	0	1	0
1	0	0	1	1	1
0	1	1	0	1	0
0	1	0	1	1	1
0	0	1	0	0	0
0	0	0	1	0	0

The SOP expansion of F is the Boolean Sum of three min terms corresponding to the three rows of this table that give the value 1


the function. That gives,

$$F(x, y, z) = x y \bar{z} + x \bar{y} \bar{z} + \bar{x} y \bar{z}$$

Truth table and circuit for AND, OR, NOT, Ex-OR, Ex-nor gates.

AND Gate: In AND Gate, the output will be 1 if and only if the inputs are 1.

A	B	$Y = A \cdot B$
1	1	1
1	0	0
0	1	0
0	0	0

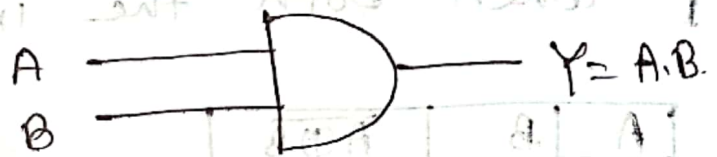

OR Gate: The output of OR gate will be 1 if one or more inputs attain the state 1.

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1



NOT Gate: The output of Not gate is the logical inversion of input.

A	Y
1	0
0	1




X-OR: The output of X-OR Gate attains 1, if exactly one of the inputs attain 1.

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0



X-NOR: The output of X-NOR gate attains 1 when both the inputs are same state.

A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

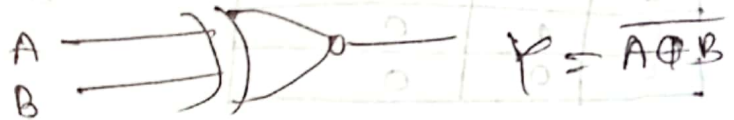


Universality of nand gate.

Nand to NOT:



$$Y = \overline{A \cdot A} = \overline{A} \quad [A \cdot A = A]$$


Nand to AND:

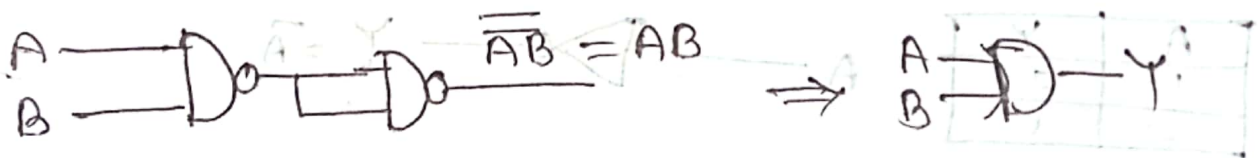

$$\text{here } Y = \overline{\overline{A \cdot B}} = A \cdot B \quad [\because \overline{\overline{A}} = A]$$

which is and gate.

Nand to OR'.

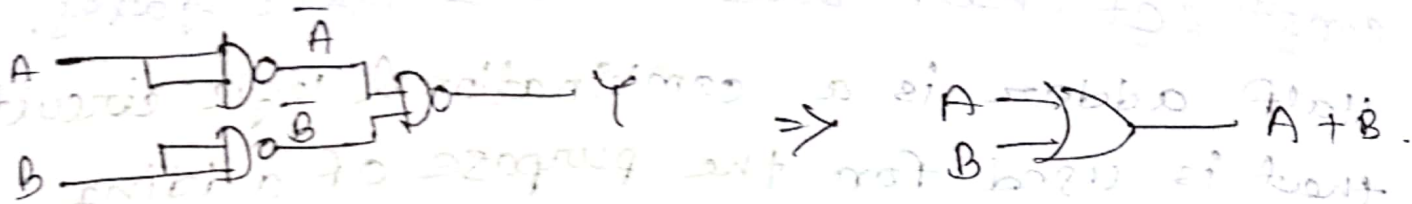

here, $Y = \overline{A \cdot B} = \overline{A} + \overline{B}$ [$\overline{A \cdot B} = \overline{A} + \overline{B}$]
 $= A + B$ [$\overline{\overline{A}} = A$]

which is or gate



Universality of OR gate: $\text{aib} \rightarrow \text{aib}$
 $\text{nor} \rightarrow \text{nor}$

NOR to NOR:



here, $\overline{A+A} = \overline{A}$ $[\because A+A = A]$

NOR to OR:



here, $\varphi(A) = \overline{\overline{A+B}} = A+B + 0[\overline{\overline{A}} = A]$

which is OR gate, DDA is

NOR to and '.




here. $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$
 $= AB$

which is AND Gate

construct half adder using logic gates.

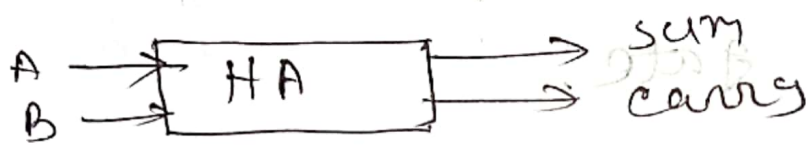Half adder is a combinational logic circuit that is used for the purpose of adding two single bit numbers. It contains 2 inputs and 2 outputs.




Block diagram.

Let's construct the truth table and simplify the expression:

A	B	Sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1
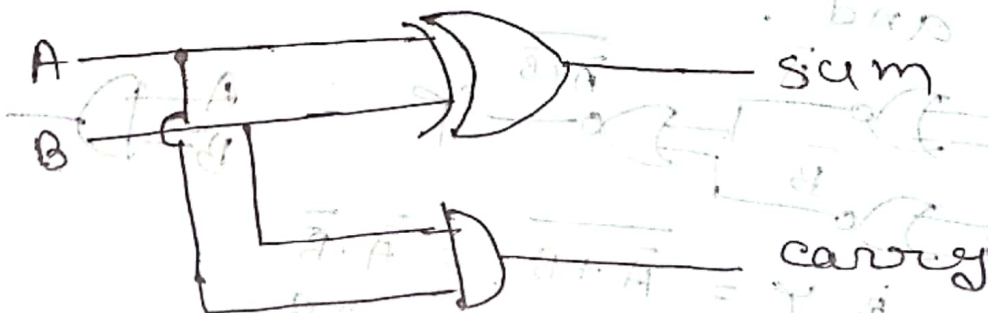
$$\therefore \text{Sum} = \bar{A}B + A\bar{B} = \text{carry} = AB \\ = A \oplus B$$



HA logic diagram

construct full adder using logic gates.


Full adder is a combinational logic circuit that is used for the purpose of adding two single bits with a carry. It contains 3 ~~lets~~ ~~can~~ inputs and 2 outputs.

Let's construct the truth table and simplify the expression:

A	B	Cin	Sum	Count
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}\therefore \text{Sum} &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in} \\ &= \bar{A}(\bar{B}C_{in} + B\bar{C}_{in}) + A(\bar{B}\bar{C}_{in} + BC_{in}) \\ &= \bar{A}(B \oplus C_{in}) + A(\overline{B \oplus C_{in}}) \\ &= A \oplus B \oplus C_{in}\end{aligned}$$
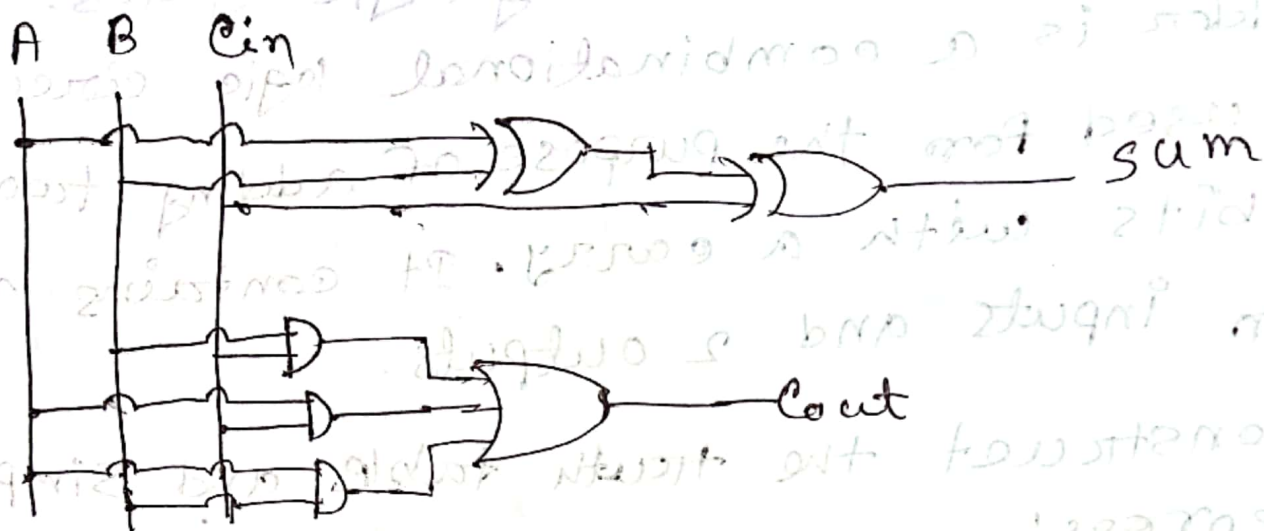
$$\begin{aligned}\text{Count} &= \bar{A}B C_{in} + A\bar{B} C_{in} + AB\bar{C}_{in} + ABC_{in} \\ &= \bar{A}B C_{in} + AB C_{in} + A\bar{B} C_{in} + AB\bar{C}_{in} + AB\bar{C}_{in} + A \\ &= BC_{in} + AC_{in} + AB\end{aligned}$$




Construct full Adder using half adder.

From, above,

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$
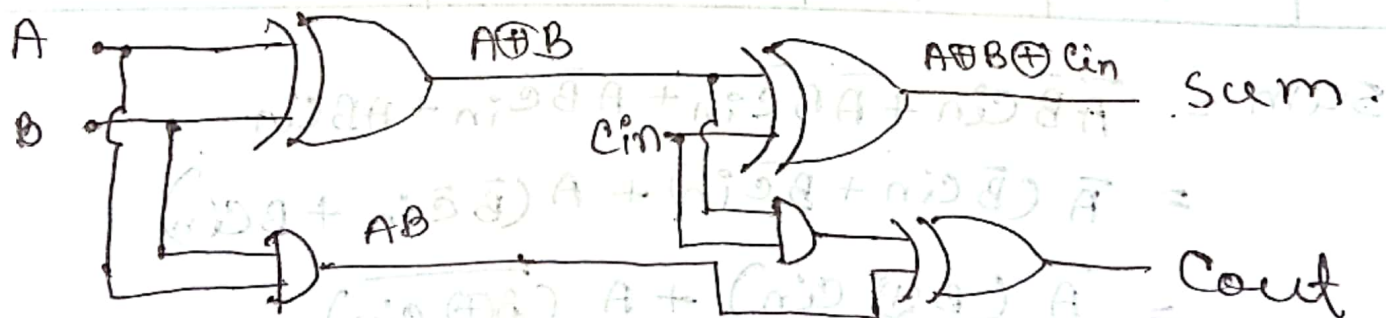
$$\begin{aligned} \text{Cout} &= \bar{A}B\text{Cin} + A\bar{B}\text{Cin} + AB\bar{\text{Cin}} + ABC\text{in} \\ &= \text{Cin}(A \oplus B) + AB \end{aligned}$$



using k-map, minimize the sop expressions:

~~(i) $ABC + \bar{B}CD + \bar{A}BC\bar{D} + ABC\bar{D}$~~

(i) $x y \bar{z} + x \bar{y} \bar{z} + \bar{x} y z + \bar{x} \bar{y} \bar{z}$

Since the expression has 3 variables, so, we need to draw $2^3 = 8$ cells.

	yz	$y\bar{z}$	$\bar{y}\bar{z}$	$\bar{y}z$
x				
x		1	1	
$\bar{x}$	1		1	

Here, we have three pairs.

$$\therefore F = \bar{x} y z + x \bar{z} + \bar{y} \bar{z}$$

(ii) $x \bar{y} z + x \bar{y} \bar{z} + \bar{x} y z + \bar{x} \bar{y} \bar{z}$

	yz	$y\bar{z}$	$\bar{y}\bar{z}$	$\bar{y}z$
x				
x	1		1	
$\bar{x}$	1			1

$$\therefore F = x \bar{y} + \bar{x} z$$

(i) $\overline{x}yz + x\overline{y}z$

	yz	$\overline{y}z$	$y\overline{z}$	$\overline{y}\overline{z}$
x				
$\overline{x}$	1	1		

$\therefore F = \overline{x}z$

(ii) $\overline{x}y\overline{z} + x\overline{y}z + \overline{x}yz + x\overline{y}\overline{z}$

	yz	$\overline{y}z$	$y\overline{z}$	$\overline{y}\overline{z}$
x		1	1	1
$\overline{x}$	1	1		1

$\therefore F = \overline{x}y + y\overline{z} + x\overline{y}\overline{z}$

(iii) $\overline{x}y\overline{z} + x\overline{y}z + \overline{x}yz + x\overline{y}\overline{z}$

	yz	$\overline{y}z$	$y\overline{z}$	$\overline{y}\overline{z}$
x		1		1
$\overline{x}$	1	1		

$\therefore F = \overline{x}z + yz + x\overline{y}\overline{z}$

(iv) $x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$

	yz	$y\bar{z}$	$\bar{y}z$	$\bar{y}\bar{z}$
x				
$\bar{x}$				

$F = \bar{y} + \bar{x}z$

(v) $x\bar{y}\bar{z} + x\bar{y}z + \bar{x}yz + \bar{x}\bar{y}z + x\bar{y}z + \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$

	yz	$y\bar{z}$	$\bar{y}z$	$\bar{y}\bar{z}$
x				
$\bar{x}$				

$F = yz + x + \bar{y}$