

INDEX

SL	Experiment Name	Page no
01	Verification of the operation of basic logic gates (AND,OR,NOT)	
02	Proof of the universality of NAND gate	
03	Verification of universality of NOR gate	
04	Verify the operation of XOR and XNOR gate using basic gate	
05	Verify the operation of Half Adder using logic gate	
06	Verify the operation of Full Adder using logic gate	
07	Verification of Half Subtractor using XOR , NOT and AND gate	
08	Verification of Full Subtractor using XOR , NOT , OR and AND gate	
09	Verification of Decoder using AND and NOT gate	
10	Verification of four input Multiplexer (MUX) using OR, AND and NOT gate	
11	Implementation of J-K flip-flop	
12	Implementation of a 4 bit Binary to Gray code converter using XOR gate	
13		