

B.Sc (HONS.) IN CSE FIRST YEAR, SECOND SEMESTER EXAMINATION, 2020

DIGITAL SYSTEMS DESIGN

[According to the New Syllabus]

Subject Code : 510221

Examination Code : 5612

Time—3 hours

Full marks—80

[N.B. The figures in the right margin indicate full marks. Answer any four questions.
Different parts of a questions must be answered sequentially.]

Marks

1. (a) Describe the main functional units of a digital computer.

5

(b) Write short notes about the following terms:

4

(i) BCD code

(ii) Unicode - 16 bit

(c) Represent the decimal number 396 in

(i) Binary form

(ii) Gray Code

(iii) Excess-3 code

(d) What are the steps actually required for processing an analog signal using digital hardware? Explain briefly.

5

2. (a) Implement the logic circuit that has the expression $X = AB(\overline{C + D})$ using only NOR and NAND gates.

6

(b) Differentiate between binary and BCD code.

3

(c) What is Boolean algebra? Explain. the Boolean function $F = A + \overline{B}C$ in a sum of minterms.

6

(d) Design a logic circuit with inputs L, M and N. So that the output P is high. Whenever the majority of inputs are high.

5

3. (a) What is setup and hold times? Explain J-k flipflop with suitable diagrams. 2+6=8


(b) How can a J-k flipflop be modified to operate as a D flipflop and a T flipflop?

6

(c) What is NAND gate latch? Explain clocked S-C flipflop with timing diagram. 2+4=6

[Please turn over]

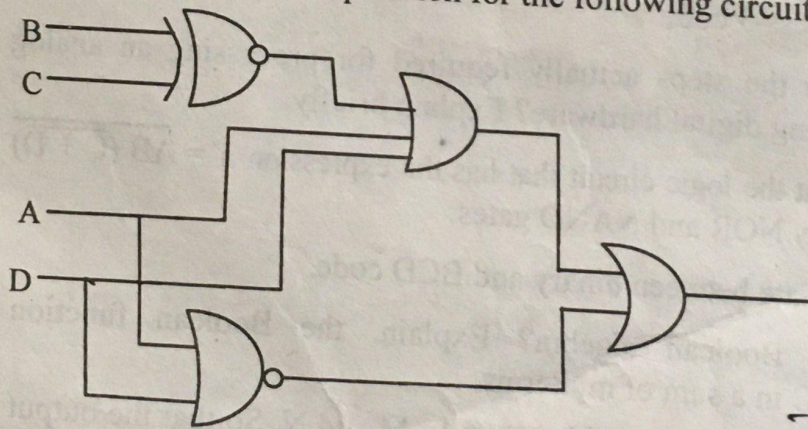4. (a) Explain the difference between a DEMUX and a MUX. 6
 (b) Design and explain four-input multiplexer. 6
 (c) What is semiconductor memory? Discuss the classification of semiconductor memory. 6
 (d) Describe static and dynamic RAM. 4
5. (a) What is Decoder? Explain 3 to 8 line Decoder with truth table and circuit diagram. 6
 (b) What is Karnaugh map? Using K-map simplify the following expression: 4
- $$F(A, B, C, D) = \sum m(1, 3, 4, 6, 8, 9, 11, 13, 15) + d(0, 2, 14)$$
- (c) Show how to wire a 74LS293 as a MOD-14 counter. 4
 (d) Design a full adder circuit using basic logic gates and explain its operations with truth table. 6
6. (a) State the purpose of analog to digital conversion. 5
 (b) Mention some applications of Decoder. 5
 (c) Explain the operation of a 4 bit R-2R ladder DAC. 6
 (d) Determine the output expression for the following circuit: 4



৩৫১এক্স

3 9 6
 0011 1001 1001
 0110 1101 1101
 0410 = 0101