

**B.Sc. (HONS.) IN CSE FIRST YEAR, SECOND SEMESTER
EXAMINATION, 2021**

DIGITAL SYSTEMS DESIGN

[According to the New Syllabus]

Subject Code : 510221


Examination Code : 5612

Time—3 hours

Full marks—80

[N.B. The figures in the right margin indicate full marks. Answer any four questions. Different part of a questions must be answered sequentially.]

- | | Marks |
|--|-------|
| 1. (a) What is analog and digital system? Write down the advantages of digital techniques. | 5 |
| (b) Convert the following numbers into given base numbers : | 6 |
| (i) $(110101)_2 = (?)_{10}$ | |
| (ii) $(129A \cdot B8C)_{16} = (?)_2$ | |
| (iii) $(225 \cdot 225)_{10} = (?)_2$ | |
| (c) Explain the method of subtraction using 2's complement method with example. | 5 |
| (d) Write short notes about the following terms : | 4 |
| (i) ASCII Code | |
| (ii) Gray Code. | |
| 2. (a) Define universal gate. Prove the universality of NAND gate and NOR gate. | 6 |
| (b) State and prove De-Morgan's theorem. | 5 |
| (c) Determine the output expression for the circuit of the following figure and simplify it using De-Morgan's theorem. | 4 |

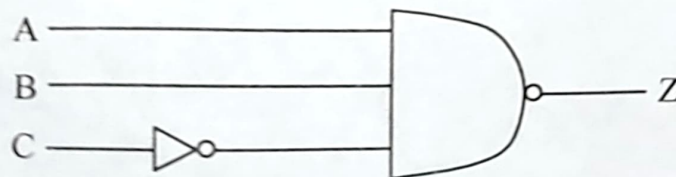

- (a) Simplify the expression.

$$Z = ABC + AB\bar{C} + (\overline{A \cdot C})$$

[Please turn over

	Marks
3. (a) What is Flip-Flop? Write down the applications of Flip-Flop.	3
(b) Explain a clocked J-K Flip-Flop.	6
(c) Define NOR gate latch? Explain clocked S-C Flip-Flop.	6
(d) Explain how J-K Flip-Flop can be converted to :	5
(i) D-type Flip-Flop	
(ii) T-type Flip-Flop.	
4. (a) To construct a Full Adder circuit by using Half-Adder circuit.	6
(b) What is Encoder? Design a Octal to Binary Encoder?	6
(c) What is ripple counter? Explain a 4-bit ripple counter with diagram.	5
(d) Write down the difference between synchronous and asynchronous.	3
5. (a) What is Demultiplexer? Sketch the logic diagram with truth table of 1 to 8 line Demultiplexer.	6
(b) What is NAND latch? Describe S-R Flip-Flop with logic diagram.	6
(c) Draw and explain 5-bit shift register.	5
(d) Mention the major drawbacks of S-R Flip-Flop.	3
6. (a) Outline the steps that take place when the CPU reads from memory.	5
(b) Differentiate between EPROM and EEPROM.	5
(c) Describe the basic operation of the digital ramp ADC.	6
(d) What is the major advantages of SAC over a digital ramp ADC?	4